

# Sensitive RF Detector for Sun Noise and other uses

Paul Wade W1GHZ ©2013

w1ghz@arrl.net


The Microwavelengths column in *QST* for July 2013 discussed Sun Noise measurement. The detector circuit I used is shown schematically in Figure 1 of the column, but there isn't room in a two-page column for a full description.

Sun noise is an increase in the noise level when pointing a reasonably high gain antenna at the sun. For most amateur antennas, the noise increase is small, only a few dB above the noise floor of a low-noise receiver.

How do we accurately detect such a small difference in noise? Certainly an S-meter is not up to the task. We can connect a VU meter to the receiver output and turn the AGC off (otherwise it will attempt to keep the noise output constant), but we will find that the meter jumps around far too much to be useful – noise is random and varies from moment to moment. We must find a way to integrate, or average, the noise output for a long enough time, perhaps one second, so that the meter holds still, but not so long that we cannot see a change as we move the antenna.

One possibility is a microwave power meter, for instance the HP 432, which detects heating of a small thermistor, and has a large meter which can easily resolve tenths of a dB. The power meter provides two benefits: the thermistor detector has a slow response time, so that the needle doesn't dance, and the scale on the meter is only about 5 dB on each range, so that tenths of a dB are easily discerned.

However, a power level in the milliwatt range is needed for a stable reading. The noise level at the antenna is on the order of -174 dBm/Hz, or -140 dBm in a typical receiver bandwidth. Using a larger bandwidth of 1 MHz (even more is better) increases the level to -114 dBm, so only 110 dB of stable gain is needed for the power meter. Part of this is provided by the microwave preamplifier and transverter, but much more is needed. At the microwave IF frequency, 144 or 432 MHz, I use a series of small amplifiers, since putting more than about 30 dB of gain in a box is asking for trouble, and filters between the amplifiers to limit the bandwidth to a few MHz. The last amplifier, the one driving the power meter, must be capable of at least 12 dB more power than the noise level, so that it can handle 99.9% of the noise peaks without clipping or saturating the amplifier. Theoretically, noise peaks may be infinite – we can't handle those, but we should be able to handle almost all the rest. A variable attenuator somewhere in the chain is useful to adjust the level for convenient meter reading.

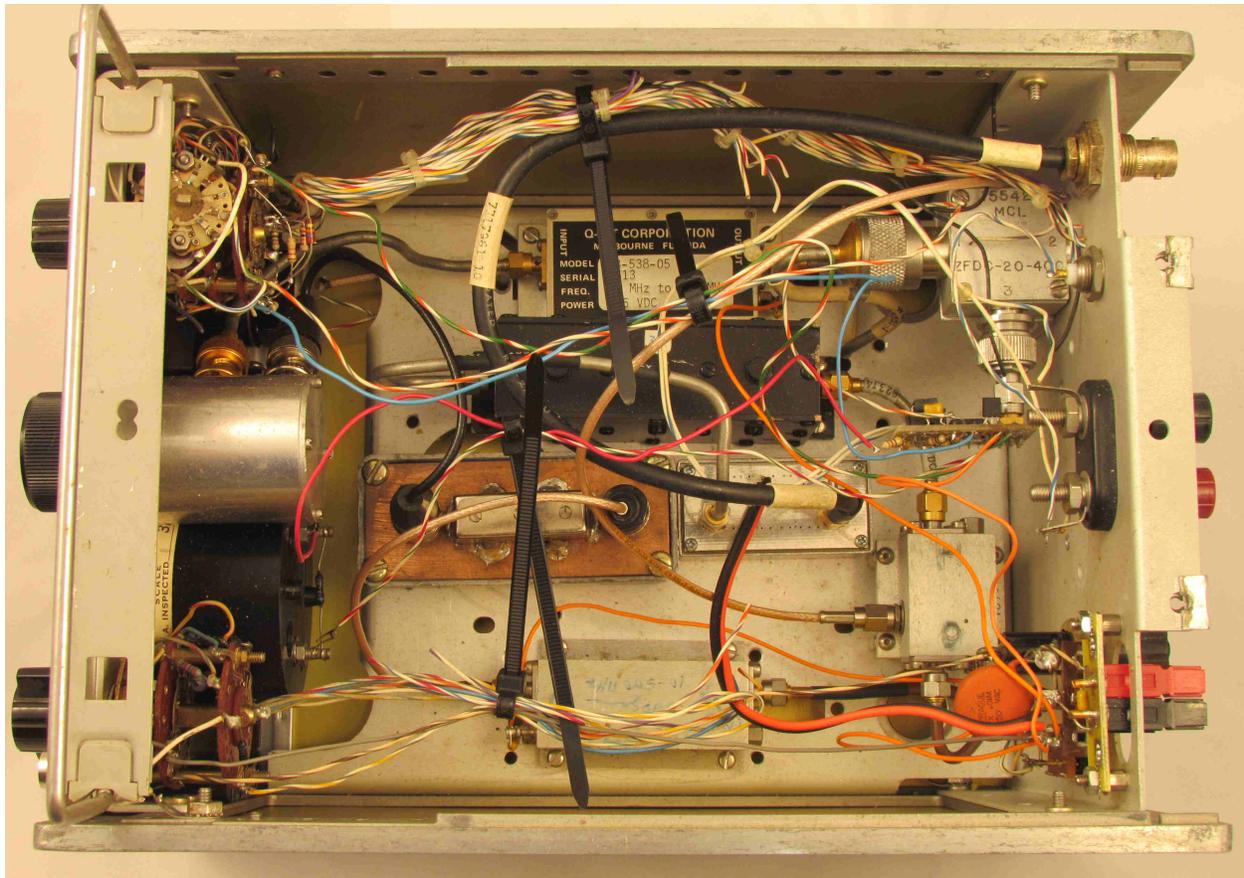


**Figure 1 - Sun Noise Detector built in defunct HP Power Meter Cabinet**

I built this system, shown in Figure 1, using a collection of surplus parts into the cabinet of an older defunct power meter, which still has the large meter movement. The front panel is visible in Figure 2 of the *QST* column, behind the dish. To make use of the existing meter movement and to eliminate the need for a separate power meter that requires AC power to operate, I included a detector circuit. The detector circuit is a power detector IC, an AD8307, whose output is linear in dB – 25 millivolts per dB.

I followed the detector with an amplifier to drive the meter movement, with enough gain so that full meter range is only 5 dB. The amplifier has a very small bandwidth, or long time constant, to average the noise and keep the needle from dancing. The voltage at the “METER ZERO” terminal is adjusted with an off-board potentiometer,  $R_z$ , to get the noise reading on scale – a ten-turn pot might make it easier to adjust. The schematic diagram of the detector and amplifier is shown in Figure 2, and a photo in Figure 3.




seen in the ExpressPCB free software is shown in Figure 4, with the top metal layer in red, the bottom metal in green, and silkscreen in light blue. Feel free to modify it for your own needs, and there is plenty of space on the Miniboard panel to add some other circuits.

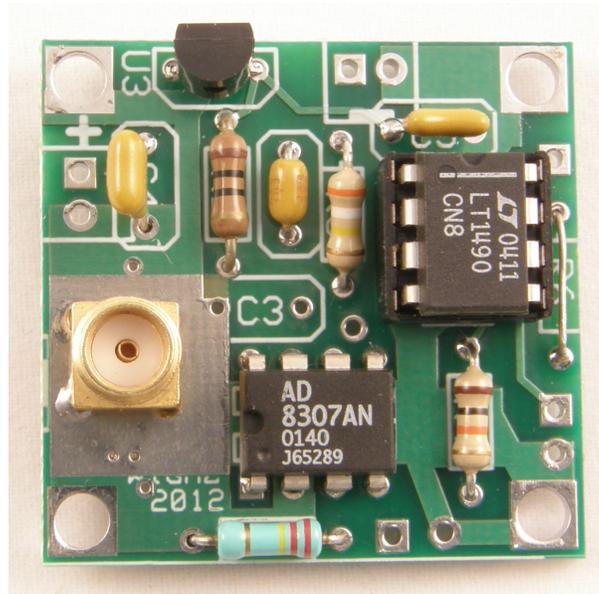

**Figure 3 – Sun Noise Detector and Amplifier**

If you haven't tried designing PC boards before, there is a short tutorial PowerPoint presentation that K3TUF and I did last year at a conference. It should be enough to get you started, and it doesn't cost anything to download the software and play with it. If you come up with something that others might find useful, please share it also.

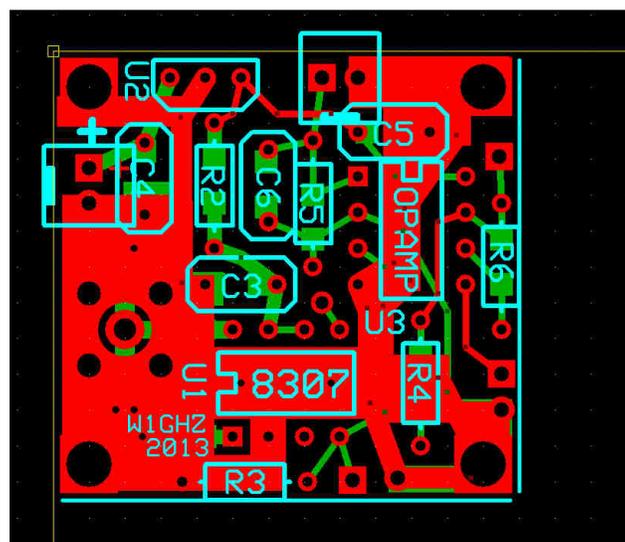

**Figure 4 – PC Board layout in ExpressPCB software**